

Computer Architecture Homework 4

Spring 2022, April

1 Boolean Algebra and Logic Gates

Question 1.1

For the following function:

bool fun(bool A, bool B) return (A == B) ? true : B;


- Write the Truth Table of it. (5 pts)
- Write the Boolean Expression of it and simplify it (as simple as possible). (10 pts)
- Draw the gate diagram that implements the boolean expression in b. (5 pts)

a.

A	B	fun(A,B)
0	0	1
0	1	1
1	0	0
1	1	1

b.
$$\text{fun}(A,B) = \bar{A}\bar{B} + \bar{A}B + AB = \bar{A} + AB = \bar{A} + B$$

c.

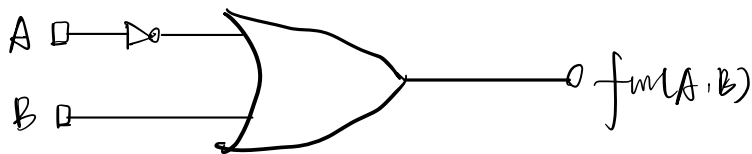


Question 1.2

a. Simplify the following Boolean Expressions (as simple as possible and show enough steps please). (15 pts)

$$\begin{aligned}
 & B(AB + A\bar{B})(\bar{A}\bar{C} + C) + \bar{C}\bar{C} + (A + \bar{B})(\bar{C}\bar{D}) \\
 = & (\cancel{AB} + A\bar{B})(\bar{A}\bar{C} + C) + \bar{C} + A\bar{C}\bar{D} + \bar{B}\bar{C}\bar{D} \\
 = & AB(\bar{A}\bar{C} + C) + \bar{C} + A(\bar{C} + \bar{D}) + \bar{B}(\bar{C} + \bar{D}) \\
 = & AB(\bar{A} + \bar{C} + C) + \bar{C} + A\bar{C} + A\bar{D} + \bar{B}\bar{C} + \bar{B}\bar{D} \\
 = & AB(\bar{A} + 1) + \bar{C} + A\bar{C} + A\bar{D} + \bar{B}\bar{C} + \bar{B}\bar{D} \\
 = & AB + \bar{C} + A\bar{C} + A\bar{D} + \bar{B}\bar{C} + \bar{B}\bar{D} \\
 = & AB + (\bar{C} + A\bar{C} + \bar{B}\bar{C}) + (A\bar{D} + \bar{B}\bar{D}) \\
 = & AB + \bar{C} + (A + \bar{B})\bar{D}
 \end{aligned}$$

$AB + \bar{C} + A\bar{D} + \bar{B}\bar{D}$
 $AB + \bar{C} + A\bar{D} + \bar{B}\bar{D}$

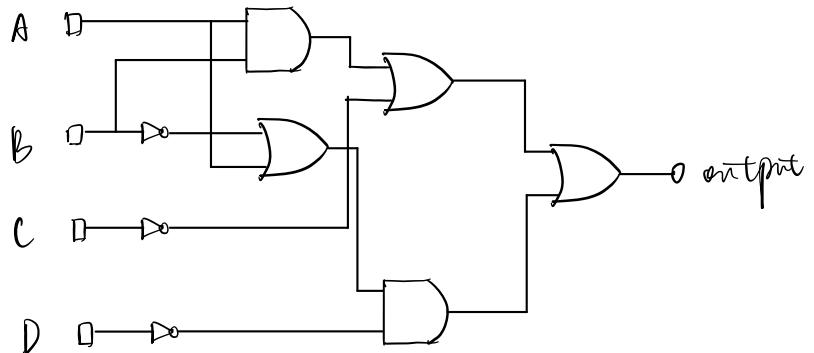
b. Draw the circuit according to the simplified boolean expression in (a). (10 pts)



2 FSM

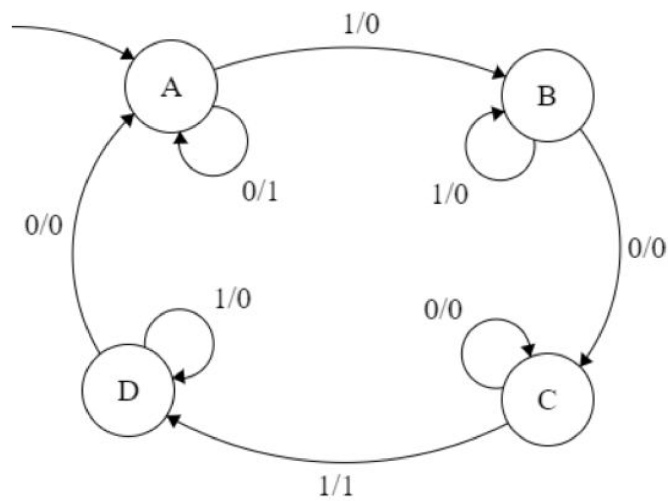Question 2

For the following Finite State Machine, fill out the remainder of the table.
(15 pts)



Input	-	1	0	0	1	1	0	0	0
Next State	A	B	C	C	D	D	A	A	A
Output	-	0	0	0	1	0	0	1	1

Table 1: Write Answer Here

